

INSTRUCTOR SOLUTION



Habib University

EE-172/CS-130/CE-222 Digital Logic and Design – Spring 2026

ID: _____

Time = 30 minutes

Quiz 03

Max Points: 20

This Quiz assesses CLO No 2 – “Apply principles of Boolean Algebra to represent and build equivalent realizations of digital logic (circuits)”

Question 1 [4 + 4 points]:


Implement the following Boolean function F , together with don't-care conditions d by finding the following for gate-level implementation: -

- Simplified SOP expression.
- Simplified POS expression.

$$F(w, x, y, z) = \sum(0, 2, 3, 8, 10, 11, 13, 14) \text{ and } d(w, x, y, z) = \sum(12, 15)$$

Note – use the 4x4 map below by marking all necessary information

a) $F = wx + x'y + x'z'$
SOP

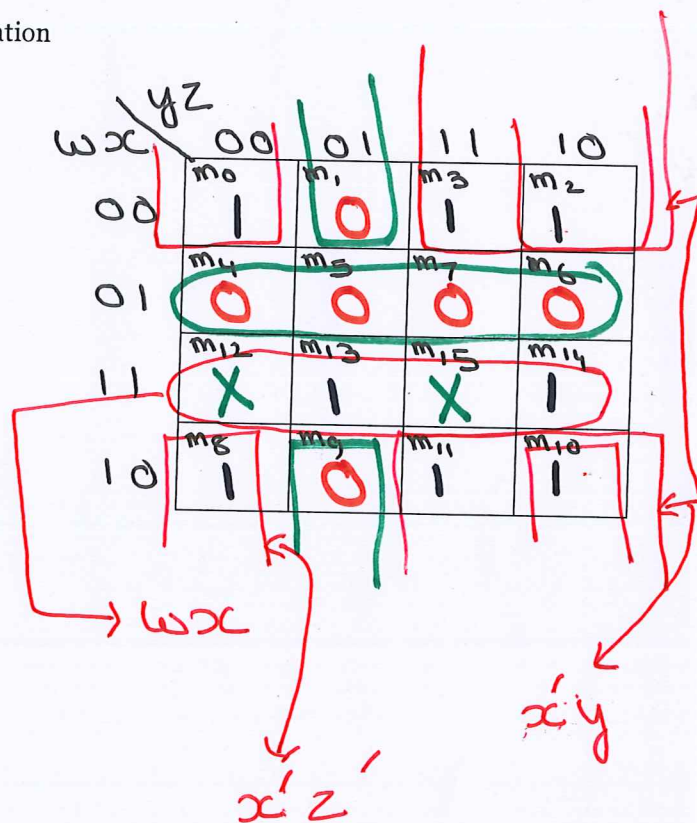


b) $F' = w'x + x'y'z$
 $\Rightarrow F = (w'x + x'y'z)'$
 $= (w'x)' \cdot (x'y'z)'$
 $F = (w + x') \cdot (x + y + z')$
 POS

Question 2 [4 + 4 points]:


- (a) Implement the following Boolean expression (expressed as POS) using NOR gates (only):

$$F = (A + B)(C + D)(E + F)$$

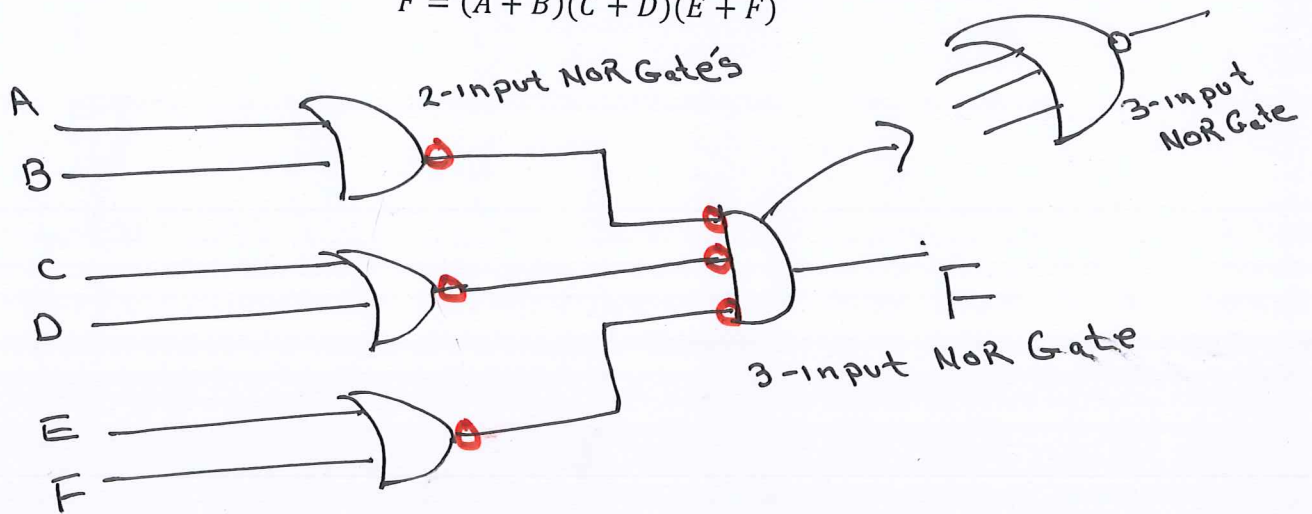

- (b) Implement the following multi-level Boolean function using NAND gates (only):

$$F = (A'C + AC')(B + D)$$

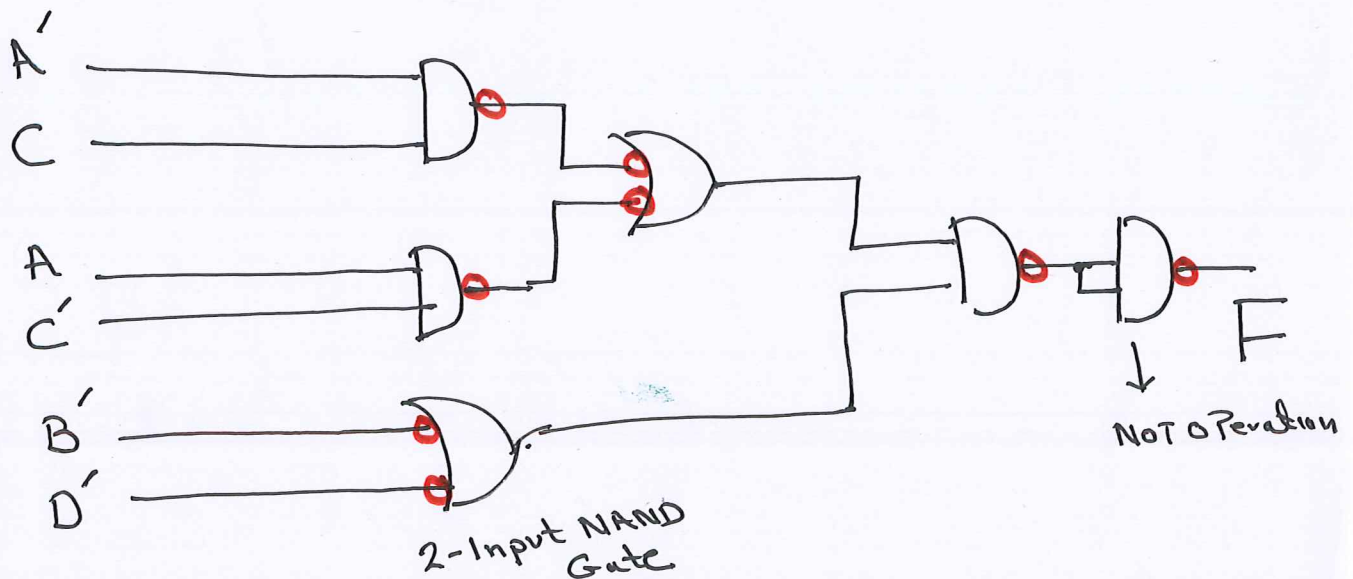


Question 3 [4 points]:

Implement a 4-input XOR function using AND, OR and NOT gates. Assume inputs as, A, B, C, D.

AB \ CD	CD			
	00	01	11	10
00	m ₀	m ₁	m ₃	m ₂
01	m ₄	m ₅	m ₇	m ₆
11	m ₁₂	m ₁₃	m ₁₅	m ₁₄
10	m ₈	m ₉	m ₁₁	m ₁₀

					4-input XOR
A	B	C	D	F	
m ₀	0	0	0	0	0
✓ m ₁	0	0	0	1	1
✓ m ₂	0	0	1	0	1
m ₃	0	0	1	1	0
✓ m ₄	0	1	0	0	1
m ₅	0	1	0	1	0
m ₆	0	1	1	0	0
✓ m ₇	0	1	1	1	1
✓ m ₈	1	0	0	0	1
m ₉	1	0	0	1	0
m ₁₀	1	0	1	0	0
✓ m ₁₁	1	0	1	1	1
m ₁₂	1	1	0	0	0
✓ m ₁₃	1	1	0	1	1
✓ m ₁₄	1	1	1	0	1
m ₁₅	1	1	1	1	0

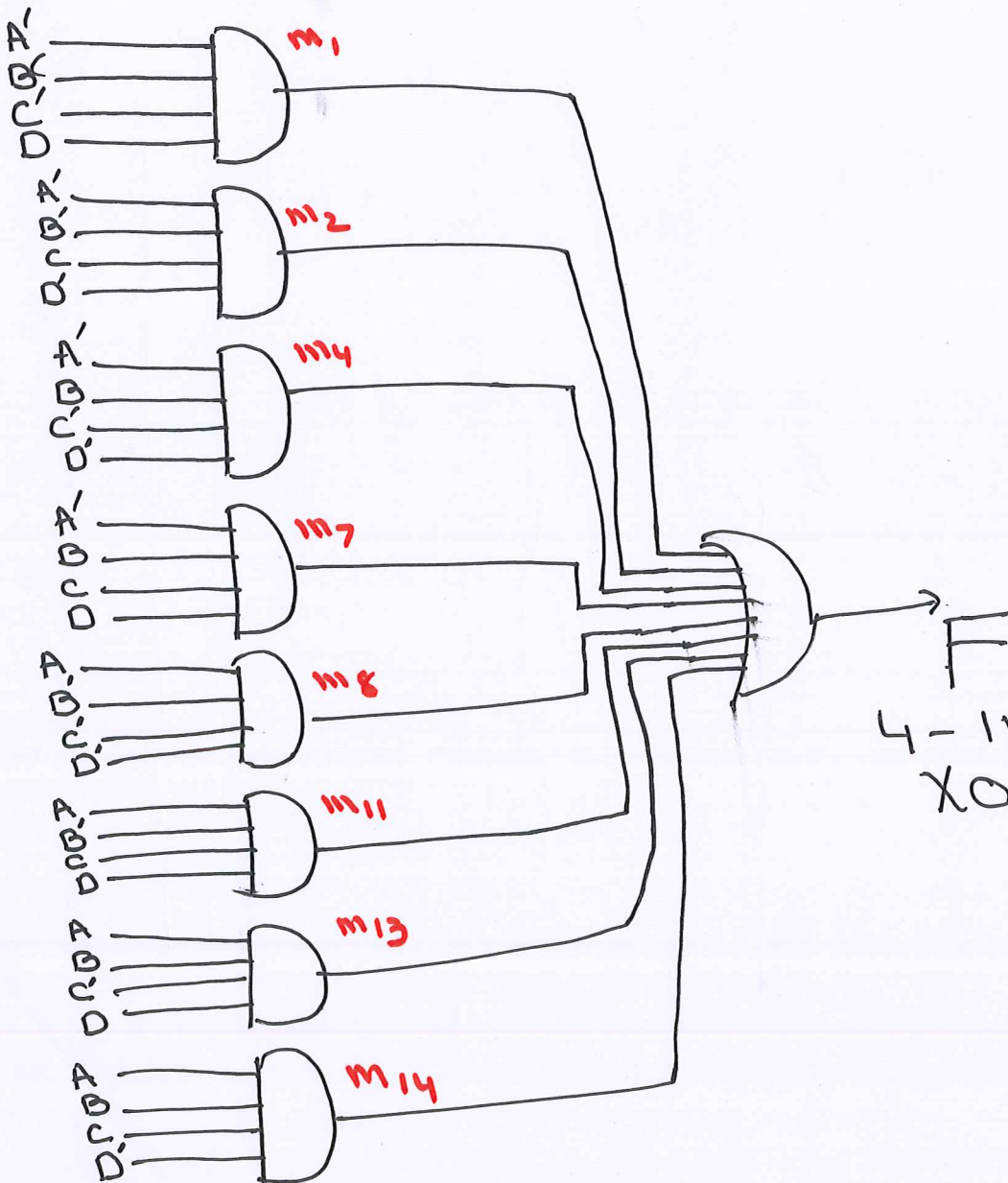

4-Input XOR Function